

UNIVERSITY OF KWAZULU-NATAL
School of Engineering

MAIN EXAMINATIONS: 2013

Subject, Course and Code: **Electronic Engineering: ENEL2ECH2**

Duration: TWO hours

Paper 1 of 1

Maximum marks: 60

Examiners: Mr. R Sewsunker (Internal)
Prof. T J O Afullo (Independent Moderator)

Instructions:

1. **Answer BOTH questions in Section A and ANY ONE question in Section B.**
 2. Show adequate work in your solutions.
 3. **No notes** of any form are allowed in the examination.
 4. Programmable calculators may be used, provided **text and formulae are removed from memory prior to the start of the examination.**
 5. Label all sketches and plots.
-

SECTION A: Answer BOTH questions in this Section.**Question A1:** [20 marks]

- (a) The circuit shown in Figure 1 uses real diodes each of which has a forward voltage drop of 0.8 Volts.
- Show with justification the assumption that both diodes are ON is incorrect. [3]
 - Determine the correct states of the diodes supporting your answers with justification. [2]

 


Figure 1

- (b) The circuit in Figure 2 is based on a real operational amplifier which has a maximum input offset voltage of 10 mV. Given that $\frac{R_2}{R_1} = 10$, determine the maximum output error voltage. [3]

 


Figure 2

- (c) The following logic problem is posed. A hydroponic tomato bed is monitored by three sensors as follows: level of nutrition, N = logic 1 provided the nutrition level is sufficient; water level, W = logic 1 provided the water level is sufficient and temperature alert, T = logic 0 if the bed temperature is within limits.
- Draw the truth table and write down the simplified logic expression for the logic function of an alarm signal, $A = f(N, W, T)$ which sounds a buzzer if either both the water and nutrition levels are low or the temperature is out of limits. [2]
 - Draw the logic circuit diagram that implements $A = f(N, W, T)$ [1]
 - Draw an alternate logic circuit diagram for $A = f(N, W, T)$ using only NAND gates. [2]

- (d) Consider the half-wave rectifier based power supply circuit shown in Figure 3, designed to have a peak-to-peak ripple voltage of 2 V.
In the circuit $v_s(t) = 20 \sin(200\pi t)$ volts, $R_{load} = 190\Omega$.

 


Figure 3

- Sketch the voltage waveform across the load resistor for one cycle of the input signal, showing the peak value. [2]
- Calculate the average value of the voltage across the load. [1]
- Given the expression for C as shown above, compute the capacitance value needed. [2]
- How would the peak-to-peak ripple voltage change if the half-wave rectifier diode in the circuit is replaced by full-wave diode-bridge based rectifier, also made up of ideal diodes? What would happen to the average value of the load current? [2]

Question A2: [20 marks]

- (a) A simple BJT amplifier is shown in Figure 4. The BJT has $\beta = 100$ and $V_{BE} = 0.7V$.

 


Figure 4

- Analyse the dc bias circuit to determine I_C and V_{CE} . [6]
- Confirm the BJT is in the correct region for amplifier operation. [1]

(b) Figure 5 shows the circuit of a filter with $L = 10\mu H$, $R = (20\pi)\Omega$.

 


Figure 5

- (i) Find the circuit transfer function, $H(f)$. [2]
 - (ii) Draw the asymptotic Bode magnitude and phase plots for the circuit. [6]
- (c) Figure 6 shows a 4-bit digital-to-analog converter (DAC) based on an operational amplifier. In the circuit if the input bit is 1, the corresponding switch is up; if the bit is 0 the switch is down. Let the binary input be represented by $b_3b_2b_1b_0$, where b_3 controls S_3 , b_2 controls S_2 , etc.

 


Figure 6

- (i) Using values of $100\text{ k}\Omega$ for R_1 , $50\text{ k}\Omega$ for R_2 , and 1 volt for V , solve for the analog output for input $b_3b_2b_1b_0 = 0110$. Assume all components of the circuit, the voltage source V and the ground connection are ideal. [3]
- (ii) The above circuit produces an analog output with $\pm 2\%$ full-scale error. Comment on the match of resolution and accuracy for this DAC. Support your answer with reason. [2]

SECTION B: Answer ANY ONE question in this Section.**Question B1:** [20 marks]

(a) Figure 7 shows a circuit based on an ideal operational amplifier and a signal used as input to the circuit.

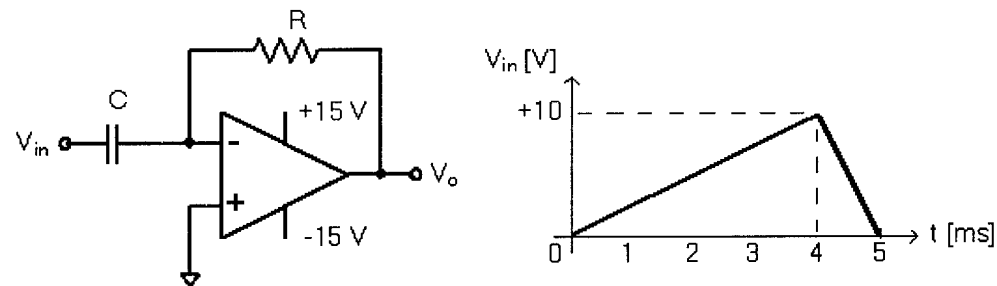


Figure 7

- Identify the circuit and from first principles solve for the output voltage in terms of the input voltage. [3]
- Given $R = 5k\Omega$, $C = 200nF$ draw the output voltage waveform for the same period of time as the input signal showing necessary calculations. [4]

(b) Figure 8 shows the complementary metal-oxide semiconductor (CMOS) transistor implementation of a particular logic function.

 


Figure 8

- Given that A and B are inputs and Z is the output, draw the equivalent circuit for each input combination based on the switch-model and show the output logic level in each case. [4]
- State what logic function this circuit performs. [1]
- Determine the output bit-stream if the input bit-streams $A=1001$ and $B=1101$ are applied to the circuit. [1]

(c) Figure 9 shows the circuit symbol of a J-K flip-flop with its function table alongside.





J	K	CLK	Q	QN
x	x	0	last Q	last QN
x	x	1	last Q	last QN
0	0		last Q	last QN
0	1		0	1
1	0		1	0
1	1		last QN	last Q

Figure 9

- (i) Show how you would connect up a few J-K flip-flops to make a 3-bit binary counter. You may use any additional combinational logic gate needed. Assume a suitable CLOCK waveform is available. [4]
- (ii) Show the count operation of your sequential logic circuit in part (i) by drawing the output waveforms. [3]

Question B2: [20 marks]

(a) The circuit shown in Figure 10 is based on ideal operational amplifiers.

 


Figure 10

- (i) Design the required resistor values so voltage source v_1 sees a voltage gain of +210 and voltage source v_2 sees a voltage gain of -150. [3]
- (ii) Assuming 1 % tolerance resistors are available to build the circuit, compute the voltage gain tolerance for each input. [2]

(b) Simplify the following logic expression using basic rules of Boolean algebra. [3]

$$Y = f(A, B) = (A + B) \cdot (\bar{A} + A \cdot B)$$

(c) Figure 11 below shows the circuit of a filter.

 


Figure 11

- (i) Apply *Thévenins* theorem to draw an equivalent circuit which has a single resistive component. [3]
- (ii) Find the circuit transfer function, $H(f)$. [3]
- (iii) Draw the asymptotic Bode magnitude and phase plots for the circuit. [6]

END OF EXAM