

EXAMINATIONS – October 2016
Main

Duration : 2H00
Max.Marks : 50
Number of Questions : 5
Number of pages : 5

Examiner : Dr.C.Venugopal
Moderator : Dr J Van Coller

Instructions:

- Answer either Part A or Part B from each question
- No notes of any form are allowed into the examinations
- Scientific calculator is allowed

QUESTION 1

Part A: External Commutation Methods

The circuit shown in Fig.1a is employing resonance commutation. The commutating capacitance is $20\mu\text{F}$ and inductance is $5\mu\text{H}$. Initial voltage across the capacitor is 230V . For a constant load current of 300A , calculate

- Conduction time of the auxiliary thyristor TA (2 Marks)
- Voltage across the main thyristor T1 when it gets commutated and (6 Marks)
- The circuit turn-off time of the main thyristor T1 (2 Marks)

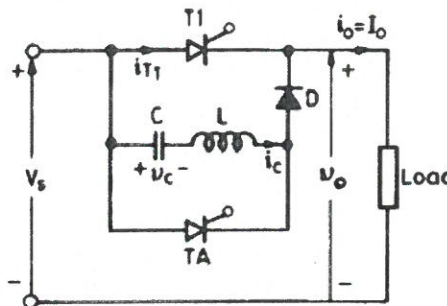


Fig. 1a

Part B: Cycloconverter Drives

The input voltage to the cycloconverter shown in Fig. 1b is 230V(rms) , 50Hz . The load resistance is 5Ω and the load inductance is 40mH . The frequency of the output voltage is 16.67Hz . If the converters are operated as semiconverters such that $0 \leq \alpha \leq \pi$ and the delay angle is α_p is $2\pi/3$. Determine

- The rms value of output voltage V_o (2 Marks)
- The rms current of each thyristor I_R (6 Marks)
- The input power factor (2 Marks)

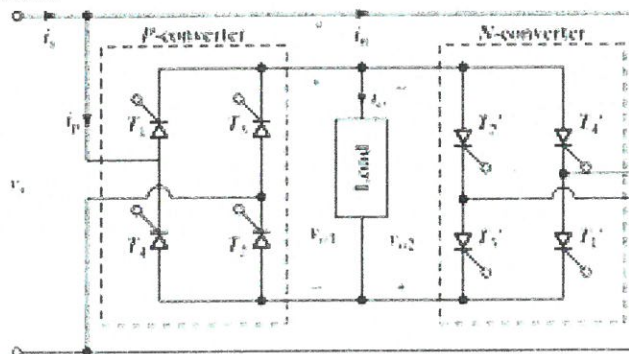


Fig.1b

QUESTION 2

Part A: Thyristor Heating, Cooling and Mounting Techniques

A power semiconductor switch has a specified thermal resistance of 0.8°C/W from junction to casing. It is mounted on a heat sink whose thermal resistance is 0.3°C/W . The thermal resistance from heat sink surface to ambient is 0.2°C/W . The switch is operating with a total power dissipation of 50W . The ambient temperature inside the cabinet in which the equipment is housed is 45°C . Determine

- The junction temperature (4 Marks)
- The temperatures of the casing and heat sink surfaces (4 Marks)
- The increased allowable power loss in the thyristor-sink combination if the heat sink temperature is brought down to 40°C by forced cooling. (2 Marks)

Part B: Dual Converters and Snubber Circuits

- A single phase dual converter is operated from a 220V , 50Hz supply. The load resistance is 15Ω . The circulating inductance is 100mH and the delay angle (α_1) of the converter 1 is 60° and delay angle (α_2) of the converter 2 is 130° . Calculate the
 - Peak circulating current (1 Mark)
 - Peak load current (1 Mark)
 - Peak current of converter 1 (1 Mark)
- A transistor is operated as a chopper switch as shown in fig.2 at a frequency f_s of 10kHz . The dc voltage of the chopper (V_s) is 220V and the load current I_L is 100A . The $V_{CE(\text{Sat})}$ is 0V for the switching times t_d of 0 , t_r of $3\mu\text{sec}$ and t_f of $1.2\mu\text{sec}$, determine
 - The values of L_s , C_s and R_s for the critically damped condition. (3 Marks)
 - The value of R_s if the peak discharge current is limited to 10% of load current (2 Marks)
 - The power loss in the RC snubber circuit neglecting the effect of inductor L_s on the voltage of the snubber capacitor C_s and the loss in diode D_s . (2 Marks)

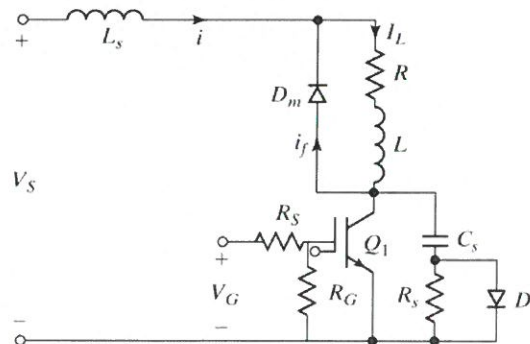


Fig.2

QUESTION 3

Part A: Multilevel Inverter

A single-phase diode-clamped multilevel inverter has 5 levels. If V_{dc} is 4kV and I_o is $50\sin(\theta - \pi/3)$. Find the

- Peak switch voltages (1 Mark)
- Peak branch diode voltages (3 Marks)
- Current ratings of diodes (6 Marks)

Part B: Inverter Harmonics

A single-phase full bridge inverter employing transistors is fed from a 220V dc supply and connected to a RLC load with $R = 6\Omega$, $L = 30\text{mH}$ and $C = 180\mu\text{F}$. The output frequency is 50Hz. Calculate

- The peak value of load current (6 Marks)
- THD of output current (4 Marks)

QUESTION 4

Part A: Synchronous Motors

A 3 phase, 5kW, 440V, 50Hz, 4 pole, Y connected synchronous motor has a stator winding resistance of 0.2Ω , synchronous reactance of 8Ω and a rated field current of 1A when operating at full load with unity power factor.

- Calculate the torque angle when operating at full load (7 Marks)
- Calculate the pull-out torque and power at pull-out torque (3 Marks)

Part B: Slip Power Controlled Drives

A 3 phase, 440V, 6 pole, 970 rpm, 50Hz, Y-connected induction motor has the following parameters referred to the stator

$$R_s = 0.2\Omega, R_r' = 0.15\Omega, X_s = X_r' = 0.4\Omega, R_d = 0.01\Omega$$

The stator to rotor turns ratio is 3.5

The motor speed is controlled by the static Scherbius drive. The drive is designed for a speed range of 30% below the synchronous speed. The maximum value of firing angle is 170° . Determine the

- Turns ratio of the transformer (2 Marks)
- Torque for a speed of 750rpm and $\alpha = 140^\circ$ (8 Marks)

QUESTION 5

PART A: Hybrid Solar and Wind Power Systems

Explain the design of hybrid solar and wind power systems with neat sketches (10 Marks)

PART B: Space Vector Modulation

Generate a reference vector, V_{ref} , that can be used by a SVPWM controlled three phase inverter to generate a three phase voltage at 65Hz with a peak voltage of 50 V. The reference vector must be generated at 3.42msecs. In what sector does the vector lie? (10 Marks)